

# Peripheral Interface IC 8255

---

## Microprocessor and Micro-Controller

Course Material – EC 403

- Functional description of Pins
- Programming the PPI
- Modes of Operation
- Interfacing with 8085

**By**

**Er. Mrs. Saraswati Saha,  
Assistant Professor, ECE Department,  
RCCIIT, Kolkata**

①


## 8255 - Programmable Peripheral Interface (PPI)

Intel has designed an IC, the 8255, with the objective of interfacing input and output devices with Intel microprocessors.

8255 is a programmable peripheral interface IC and is a multi-port input/output device. There are 24 I/O pins, which may be individually programmed in 2 groups of 12 and used, in 3 major modes of operation. The two groups of 12 I/O lines are called Group A and Group B.

Each group contains a subgroup of eight-bit port and a subgroup of four-bit port.

 This IC has three eight-bit ports: Port A ( $PA_7-PA_0$ ), Port B ( $PB_7-PB_0$ ) and Port C ( $PC_7-PC_0$ ). The Port C is divided into subgroups such as Port C upper ( $PC_7-PC_4$ ), and Port C lower ( $PC_3-PC_0$ ). Group A consists of Port A and Port C upper. Group B consists of Port B and Port C lower.



\* 8255 is a 40-pin IC package and operates on a single +5V dc supply.

### Functional description of pins

- 1) Port A (8-bit I/O pins)
- 2) Port B (8-bit I/O pins)
- 3) Port C (8-bit I/O pins)
- 4)  $D_7-D_0$  (Bidirectional 8-bit databus)
- 5)  $\overline{CS}$  (Chip select pin which is active low)
- \* 9)  $V_{cc}$  (+5V dc) & GND.

(6)  $\overline{RD}$  (Read) &  $\overline{WR}$  (write) Control signals

(7) RESET

(8)  $A_0-A_1 \rightarrow$  are normally connected to the least significant bits of the add. bus  $A_0$  and  $A_1$  and are used to select ports and control word register (CWR)



Scan

has been 'interfaced' to three I/O devices using the 8255 as a temporary storage space. Thus, the 8255 has three sets of '8-bit parallel ports', which act as intermediary between a processor and a number of I/O devices. Note that in all cases the I/O devices used have only 8-bit data capability – so, only the lower data lines D0-D7 are connected to the 8255.

However, it is a 'programmable chip' as are all the chips we will learn in the next two chapters as well. Keep in mind that these 'interfacing chips' do not have any 'processing' capability. They can only be made to act in the way we want to by 'programming' it using the instructions of 8086 (i.e., the processor to which it is connected). However, they have the hardware to do the special functions that are needed for each specific purpose. Programming interfacing chips entails writing of 'control words' in their control command registers. We will learn this idea, starting with the 8255.

### 9.2.1 | Pin Configuration and Internal Block Diagram

Figure 9.3 shows the pin configuration of the DIP (dual-in-line) version of the chip. We see that it has 40 pins, which consist of three 8-bit ports named Port A (PA), Port B (PB) and Port C (PC), each of which can be programmed as input or output ports. Figure 9.4 shows the internal block diagram of the chip. It is seen to consist of various functional blocks, and let us take a quick look at each of the blocks.

**Data Bus Buffer** There is a three state bi-directional 8-bit buffer which is used to interface the chip to the data bus of the system. Upon execution of the processor's input or output instructions, data and control/status words are received or transmitted by the buffer.

**Read/Write Control Logic** It manages all data transfer between the chip and the processor on accepting control signals from the control and address buses of the system.

 


Figure 9.3 | Pin diagram of 8255

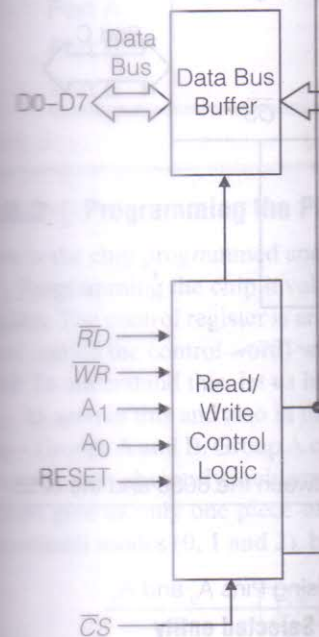


Figure 9.4 | Internal block diagram of 8255

**Group A and B Controls** Functions of the chip are controlled by two control words. They have their corresponding control registers. The way the chip is to act is determined by these control words, which can be written to and read from the chip. The chip is connected to the data bus of the 8086. The  $\overline{RD}$  and  $\overline{WR}$  signals are connected to the chip from the 8086. If this chip (which has only an eight-bit address, only the lower 8 bits of the address are involved in the address decoding. Otherwise, 16 address lines may be involved in the address decoding, which is greater than 16 bits.) Any two pins  $A_0$  and  $A_1$  of the 8255 are connected to the processor with this chip, and each one needs a control signal. The combinations of these two lines



③

Scan

as a temporary storage space which act as intermediary between the I/O devices used. The 8255 PPI has 8 pins (PA0-D7) are connected to the 8255. We will learn in the next two chapters that the 8255 does not have any 'processor' (it is connected to the processor). However, we need to program it. We need to write 'control words' in their control register to control the 8255.

ram

in-line) version of the chip. We named Port A (PA), Port B (PB) as input or output ports. Figure 9.4 shows the internal block diagram of the 8255. It consists of various functional blocks. A Data Bus Buffer is used to interface the processor's input or output data bus (D0-D7) with the internal data bus. The Read/Write Control Logic block receives control signals (RD, WR, A1, A0, RESET) and manages the internal data flow.

between the chip and the system address buses of the system.



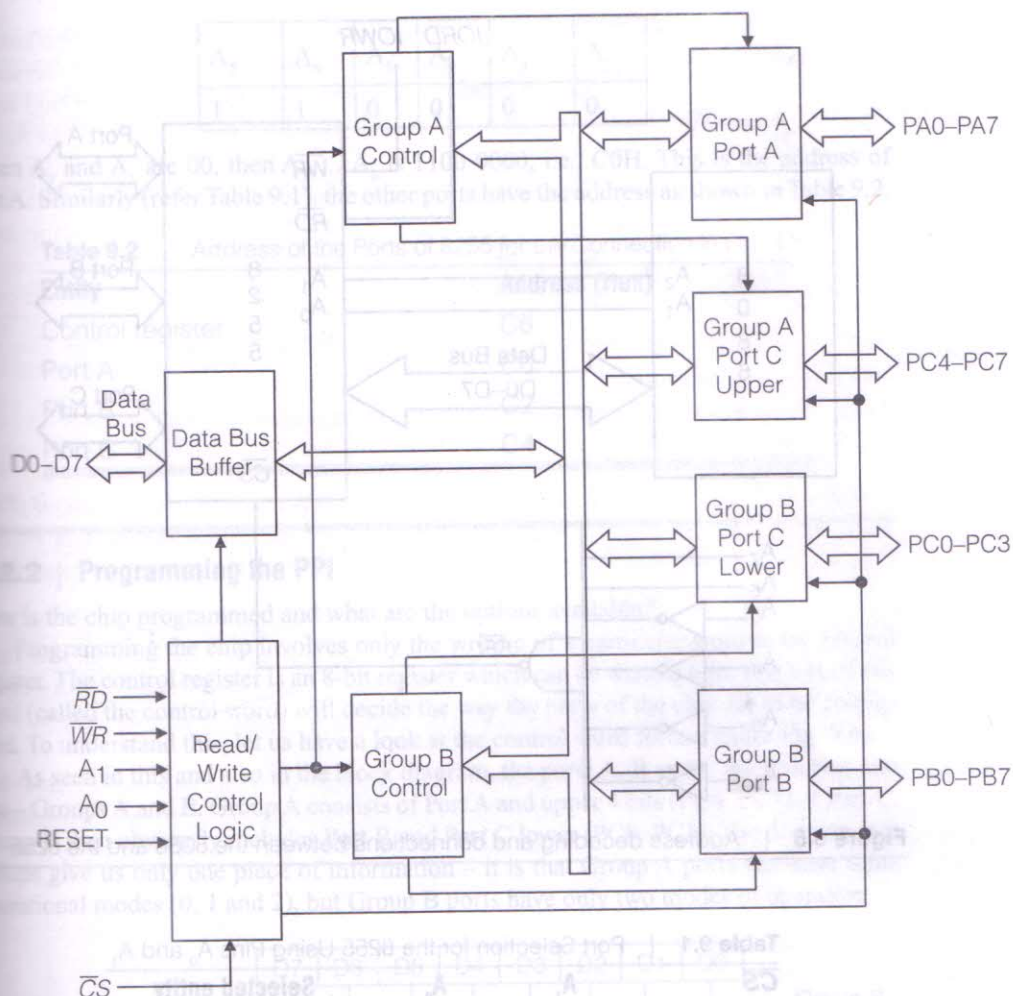


Figure 9.4 | Internal block diagram of the 8255

**Group A and B Controls** Functionally, this chip has been divided as Group A and B and they have their corresponding controls. We will soon see what this grouping is intended for. The way the chip is to act is decided by a register called the control/status register, which can be written to and read from. Now see a typical connection between the 8086 and an 8255 in Fig. 9.5. The lower data lines of the chip can be connected to 8 bits of the data bus of the 8086. The  $\overline{RD}$  and  $\overline{WR}$  are connected to the  $\overline{IORD}$  and  $\overline{IOWR}$  generated from the 8086. If this chip (which is viewed as an I/O port by the processor) is to have only an eight-bit address, only the lower 8 lines of the address lines of the processor need to be involved in the address decoding process, which causes the  $\overline{CS}$  line to be activated. Otherwise, 16 address lines may be used. (Recollect that no I/O port can have an address greater than 16 bits.) Any two address pins of the processor are to be connected to the pins  $A_0$  and  $A_1$  of the 8255. This is because there are four separate entities associated with this chip, and each one needs a unique address. This is achieved by the four possible combinations of these two lines, as shown in Table 9.1.

 

#### ④ Schematic pin diagram of 8255.

 

If we see the internal structure of the IC, we will find that, in addition with the three 8-bit I/O ports, there is another register called control register or control word register (CWR).

To identify the 3 ports and control register, the 8255 uses two address lines —  $A_0$  and  $A_1$ . These lines get their signals from the 8085 processor address bus. The identification of the ports and register ~~are~~ based on  $A_0$  and  $A_1$ . is given in Table :

$A_1$	$A_0$	selected entity
0	0	Port A
0	1	Port B
1	0	Port C
1	1	Control register.

**Programming the PPI** Programming the chip involves only the writing of a particular word to the Control register.

The control register is an 8-bit register which can be written into. The bits of this word (called the control word) will decide the way the ports of the chip are to be configured. To understand this, let us have a look at the control word format.




## Bit Assignment of the Control word.


(5)

First, look at  $D_7$  bit. It suggests the options of I/O mode or BSR (bit set/reset) mode. I/O mode is the normal mode of operation and BSR is a special mode catering to port C alone.

Operating modes.

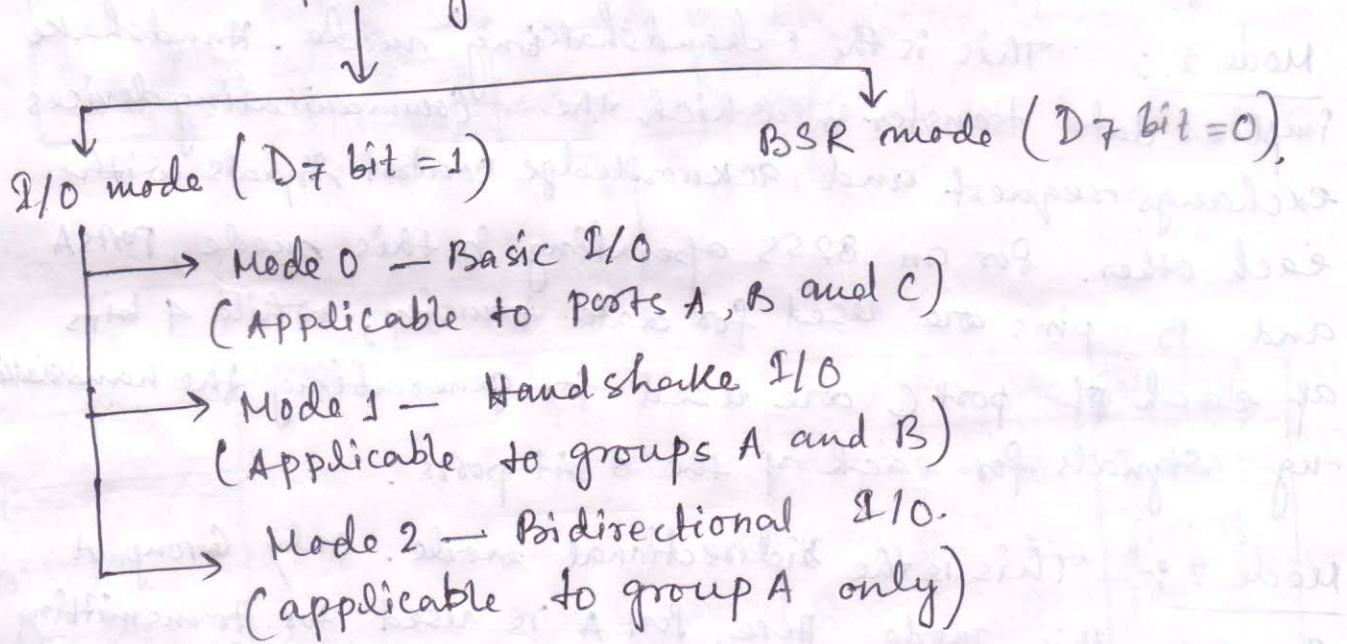

## I/O Control word format of 8255

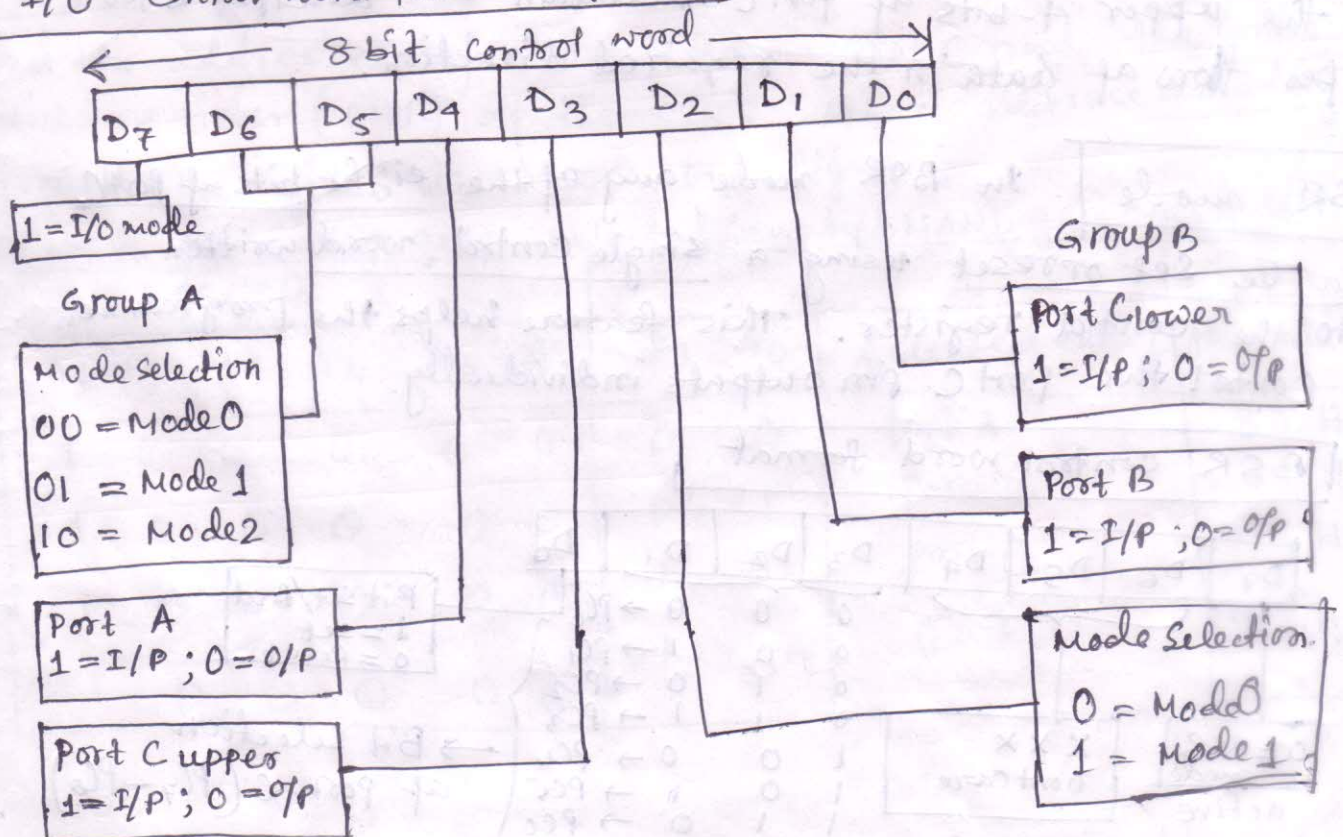



## Modes of Operation

⑥


Mode 0 :- This is the simplest and most widely used mode. In this mode, the two 8-bit ports A and B and the 4-bit ports Port C upper and Port C lower may be used independently. Here, data is simply taken in from an I/P port or given to an O/P port.

Mode 1 :- This is the 'handshaking' mode. Handshake implies data transfer in which the communicating devices exchange request and acknowledge control signals with each other. For an 8255 operating in this mode, ports A and B pins are used for data transfer, while 4 bits of each of port C are used for generating the handshaking signals for each of the 8-bit ports.

Mode 2 :- This is the bidirectional mode. Only Group A can use this mode. Here, Port A is used for transmitting as well as receiving data. Handshaking signals generated by the upper 4-bits of Port C maintain bus discipline for proper flow of data in the required direction.



BSR mode In BSR mode, any of the eight bits of Port C can be set or reset using a single control word written into the control register. This feature helps the programmer to control the Port C pin outputs individually.

### BSR control word format

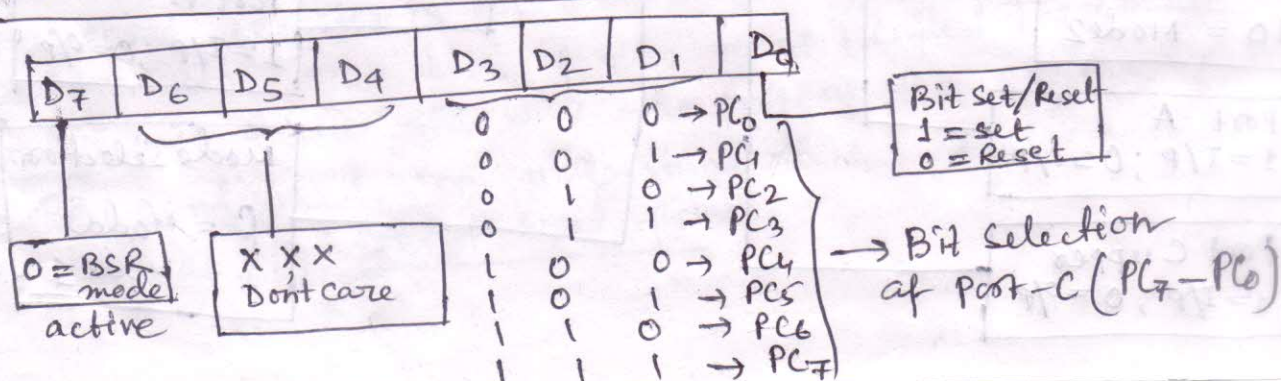


 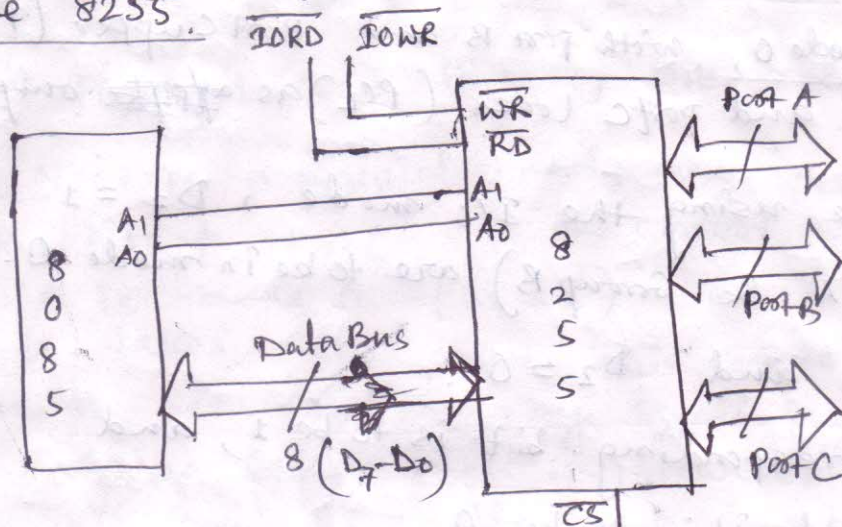
# \* Address decoding and connections between the 8085 and the 8255.



$\overline{CS}$	A1	A0	Selected entity
0	0	0	Port A
0	0	1	Port B
0	1	0	Port C
0	1	1	CWR

## Example 1 :-

Find the addresses of Port A, Port B, Port C and the Control word register (CWR) of the 8255 whose address decoding circuitry is given in the above figure.

\* (when the chip gets selected/enabled NAND gate output should be 0)

$\overline{CS} = 0$								selected entity	Port Address
A7	A6	A5	A4	A3	A2	A1	A0		
1	0	0	0	0	0	0	0	Port A	80 H
1	0	0	0	0	0	0	1	Port B	81 H
1	0	0	0	0	0	1	0	Port C	82 H
1	0	0	0	0	0	1	1	CWR	83 H




**Example 12** Design the control word to configure the ports of an 8255 chip in mode 0, with port B and port C upper (PCU) as inputs and port A and port C lower (PCL) as ~~inputs~~ outputs.

Ans. Since we are using the I/O mode,  $D_7 = 1$   
 Both groups (Group A & Group B) are to be in mode 0.  
 Hence,  $D_6 D_5 = 00$  and  $D_2 = 0$ .  
 For input, the corresponding bit is to be 1, and  
 for output, it is to be 0.

Since port A is to be an o/p port,  $D_4 = 0$   
 Since port C<sub>U</sub> is to be an ~~I/P~~ port,  $D_3 = 1$   
 Since port B is to be an I/P port,  $D_1 = 1$   
 Since port C<sub>L</sub> is to be an o/p port,  $D_0 = 0$ .

Thus the control word is 8AH.

 

Imp: The following program instructions will configure the control word of the 8255.

```

MVI A, 8AH ; Load the control word in the Accumulator.
OUT 83H ; Transfer it to the control register of the
          8255. (83H is the port address
                of the control word register.)
    
```

\* So the program for initializing the 8255 and outputting data available in port B to port A is given below:

```

MVI A, 8AH
OUT 83H
IN 80H ; Get data from port B to the accumulator
OUT 80H ; Move it to port A.
    
```



Example 3 write the BSR control words for the following cases :

(9)

- (i) PC<sub>0</sub> to be Set (ii) PC<sub>7</sub> to be reset (iii) PC<sub>1</sub> to be set (iv) PC<sub>7</sub> to be set

Ans [This is a special mode and is applicable only for the bits of port C. In the control word format, if the MSB is made 0 ( $D_7 = 0$ ), the BSR (bit set/reset) mode takes effect. In this mode, any bit of port C can be set or reset by specifying the bit which has to be set or reset. However, at a time, only one bit can be addressed - and that bit is to be either set or reset. The corresponding control word has to be decided and moved to the control register (CWR).]

Solution:-

D<sub>7</sub> D<sub>6</sub> D<sub>5</sub> D<sub>4</sub> D<sub>3</sub> D<sub>2</sub> D<sub>1</sub> D<sub>0</sub>

i) PC<sub>0</sub> to be Set: 0 X X X 0 0 0 1 = 01H  
Considering 'X' cases as '0'.

ii) PC<sub>7</sub> to be reset: 0 0 0 0 1 1 1 0 = 0EH

iii) PC<sub>1</sub> to be Set: 0 0 0 0 0 0 1 1 = 03H

iv) PC<sub>7</sub> to be set: 0 0 0 0 1 1 1 1 = 0FH

\* Here D<sub>0</sub> = 1 means Set ; & D<sub>0</sub> = 0 means reset

\* In the BSR mode port C should be in output mode.

Imp Q:- Generate a square pulse having 50% duty cycle in BSR mode using PC<sub>7</sub> pin.

- Steps:
- 1) write a delay subroutine using Reg. Pair.
  - 2) Configure the 8255 in mode 0, considering all the ports as in output mode [Control word will be 80H]
  - 3) Then write the control word to set PC<sub>7</sub> pin & to reset PC<sub>7</sub> pin.



main  
Program:-

MVI A, 80H ; Load control word into accumulator  
OUT CWR ; to configure 8255 in mode 0.  
and all ports are in off mode.

loop: MVI A, 0FH ; Control word to set the  
OUT CWR ; PC7 pin.

CALL DELAY

MVI A, 0EH ; Control word to reset the  
OUT CWR ; PC7 pin,

CALL DELAY ; [CWR <sup>Give</sup> portAddr]

JMP loop

Subroutine prog:

Delay  
prog. using  
Reg. pair.

Remarks:- You will get a square pulse  
at pin PC7.

50% duty cycle means: on and  
off time of the pulse will be of  
equal width.