

19. (a) A student is unable to see the words written on the blackboard placed at a distance of approximately 5 m from him clearly. Name the defect of vision the student is suffering from. State the possible causes of this defect and explain in brief the method of correcting this defect.
- (b) Why does the Sun appear reddish during sunrise and sunset ? Will this phenomenon be observed by an astronaut on the moon ? Give reasons to justify your answer.


5

Chapter 12 : *Electricity*

1. When a 4V battery is connected across an unknown resistor there is a current of 100 mA in the circuit. The value of the resistance of the resistor is:
- i) 4Ω
 - ii) 40Ω
 - iii) 400Ω
 - iv) 0.4Ω
2. Unit of electric power may also be expressed as:
- i) volt-ampere
 - ii) kilowatt-hour
 - iii) watt-second
 - iv) joule-second
3. At the time of short circuit, the electric current in the circuit :
- | | |
|---------------------------|-----------------------|
| (a) vary continuously | (b) does not change |
| (c) reduces substantially | (d) increases heavily |
4. Two bulbs of 100 W and 40 W are connected in series. The current through the 100 W bulb is 1 A. The current through the 40 W bulb will be :
- | | |
|-----------|-----------|
| (a) 0.4 A | (b) 0.6 A |
| (c) 0.8 A | (d) 1 A |

5. (a) Write the mathematical expression for Joule's law of heating.
 (b) Compute the heat generated while transferring 96000 coulomb of charge in two hours through a potential difference of 40 V. 3

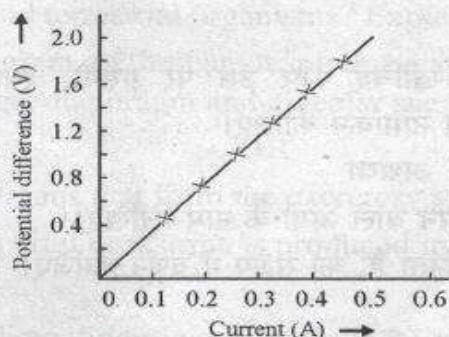
6. A V-I graph for a nichrome wire is given below. What do you infer from this graph? Draw a labelled circuit diagram to obtain such a graph. 3



7. (i) Consider a conductor of resistance ' R ', length ' L ', thickness ' d ' and resistivity ' ρ '. Now this conductor is cut into four equal parts. What will be the new resistivity of each of these parts? Why? 5
 (ii) Find the resistance if all of these parts are connected in:
 (a) Parallel
 (b) Series
 (iii) Out of the combinations of resistors mentioned above in the previous part, for a given voltage which combination will consume more power and why?


8. The maximum resistance which can be made using four resistors each of $2\ \Omega$ is
 (a) $2\ \Omega$
 (b) $4\ \Omega$
 (c) $8\ \Omega$
 (d) $16\ \Omega$ 1

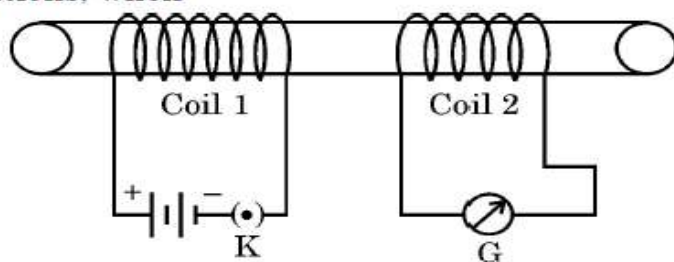9. Two coils of insulated copper wire are wound over a non-conducting cylinder as shown. Coil 1 has comparative large number of turns. State your observations, when



- (i) Key K is closed.
 (ii) Key K is opened.
 Give reason for each of your observations. 3

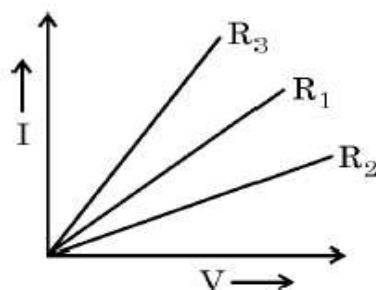10. A student plots V-I graphs for three samples of nichrome wire with resistances R_1 , R_2 and R_3 . Choose from the following the statement that holds true for this graph.



- (a) $R_1 = R_2 = R_3$
 (b) $R_1 > R_2 > R_3$
 (c) $R_3 > R_2 > R_1$
 (d) $R_2 > R_1 > R_3$

1

11. (a) Find the ratio of resistances of two copper rods X and Y of lengths 30 cm and 10 cm respectively and having radii 2 cm and 1 cm respectively.
 (b) A current of 500 mA flows in a series circuit containing an electric lamp and a conductor of $10\ \Omega$ when connected to 6 V battery. Find the resistance of the electric lamp.

5

12. The maximum resistance which can be made using four resistors each of resistance $\frac{1}{2}\ \Omega$ is

- (a) $2\ \Omega$
 (b) $1\ \Omega$
 (c) $2.5\ \Omega$
 (d) $8\ \Omega$


1

13. A cylindrical conductor of length ' l ' and uniform area of cross section ' A ' has resistance ' R '. The area of cross section of another conductor of same material and same resistance but of length ' $2l$ ' is

- (a) $\frac{A}{2}$
 (b) $\frac{3A}{2}$
 (c) $2A$
 (d) $3A$

1

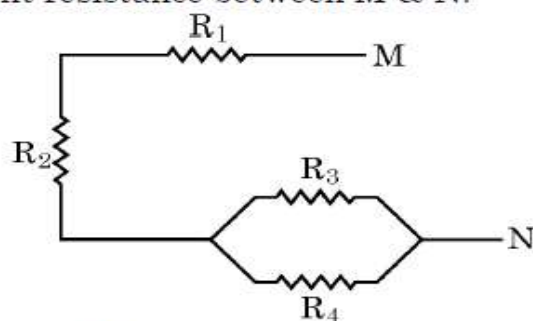14. (a) For the combination of resistors shown in the following figure, find the equivalent resistance between M & N.



- (b) State Joule's law of heating.
(c) Why we need a 5 A fuse for an electric iron which consumes 1 kW power at 220 V ?
(d) Why is it impracticable to connect an electric bulb and an electric heater in series ?

5

15. If a person has five resistors each of value $\frac{1}{5} \Omega$, then the maximum resistance he can obtain by connecting them is

1

- (A) 1Ω
(B) 5Ω
(C) 10Ω
(D) 25Ω

16. The resistance of a resistor is reduced to half of its initial value. In doing so, if other parameters of the circuit remain unchanged, the heating effects in the resistor will become

1

- (A) two times.
(B) half.
(C) one-fourth.
(D) four times.

17. Draw a schematic diagram of a circuit consisting of a battery of 3 cells of 2 V each, a combination of three resistors of $10\ \Omega$, $20\ \Omega$ and $30\ \Omega$ connected in parallel, a plug key and an ammeter, all connected in series. Use this circuit to find the value of the following :

- (a) Current through each resistor
- (b) Total current in the circuit
- (c) Total effective resistance of the circuit

5

18. Two identical resistors, each of resistance $15\ \Omega$, are connected in (i) series, and (ii) parallel, in turn to a battery of 6 V. Calculate the ratio of the power consumed in the combination of resistors in each case.

5

19. A cylindrical conductor of length ' l ' and uniform area of cross-section ' A ' has resistance ' R '. Another conductor of length $2.5\ l$ and resistance $0.5\ R$ of the same material has area of cross-section

1

- (A) $5\ A$
- (B) $2.5\ A$
- (C) $0.5\ A$
- (D) $\frac{1}{5}\ A$

20. (a) Two lamps rated 100 W, 220 V and 10 W, 220 V are connected in parallel to 220 V supply. Calculate the total current through the circuit.
- (b) Two resistors X and Y of resistances $2\ \Omega$ and $3\ \Omega$ respectively are first joined in parallel and then in series. In each case the voltage supplied is 5 V.
- (i) Draw circuit diagrams to show the combination of resistors in each case.
 - (ii) Calculate the voltage across the $3\ \Omega$ resistor in the series combination of resistors.

5

21. Two resistors A and B of resistances $10\ \Omega$ and $40\ \Omega$ respectively are first joined in series and then in parallel with two terminals of a battery. In each case the voltage applied is 5 V.

- (a) Find the ratio of currents through the resistors A and B (i.e. I_A/I_B) in each case.
- (b) Find the ratio of voltages across the resistors A and B (i.e. V_A/V_B) in each case.
- (c) Find the heat produced each second in the series combination of resistors.

5

22. (a) Define the term Potential Difference and state its SI unit.

(b) Name a device that helps to (i) maintain a potential difference across a resistor, and (ii) change current flowing through a resistor.

(c) Calculate the (i) highest, and (ii) lowest resistance that can be obtained by the combination of three resistors of resistances $20\ \Omega$, $30\ \Omega$ and $60\ \Omega$.

5